

$$f = 80 \text{ Hz}$$

$$R_b = 1200 \, \Omega$$

$$R_a = 1200 \, \Omega$$

$$C = \frac{1,44}{(R_a + 2 \cdot R_b) \cdot f} = \frac{1,44}{(1200 \, \Omega + 2 \cdot 1200 \, \Omega) \cdot 80 \text{ Hz}} = 5 \, \mu\text{F}$$

$$T_H = 0,69 \cdot (R_a + R_b) \cdot C = 0,69 \cdot (1200 \, \Omega + 1200 \, \Omega) \cdot 5 \, \mu\text{F} = 8,28 \text{ ms}$$

$$T_L = 0,69 \cdot R_b \cdot C = 0,69 \cdot 1200 \, \Omega \cdot 5 \, \mu\text{F} = 4,14 \text{ ms}$$

$$D = \frac{T_H}{T_H + T_L} \cdot 100 = \frac{8,28 \text{ ms}}{8,28 \text{ ms} + 4,14 \text{ ms}} \cdot 100 = 66,67$$

